

## **Circuit Theory and Electronics Fundamentals**

Department of Electrical and Computer Engineering, Técnico, University of Lisbon

T2: RC Circuit Analysis


Hugo Tavares dos Santos, 86639  
Ricardo Esteves Rodrigues, 95841, n.º95821  
Víctor Negrini Liotti, n.º95839

April 5, 2021

## Contents
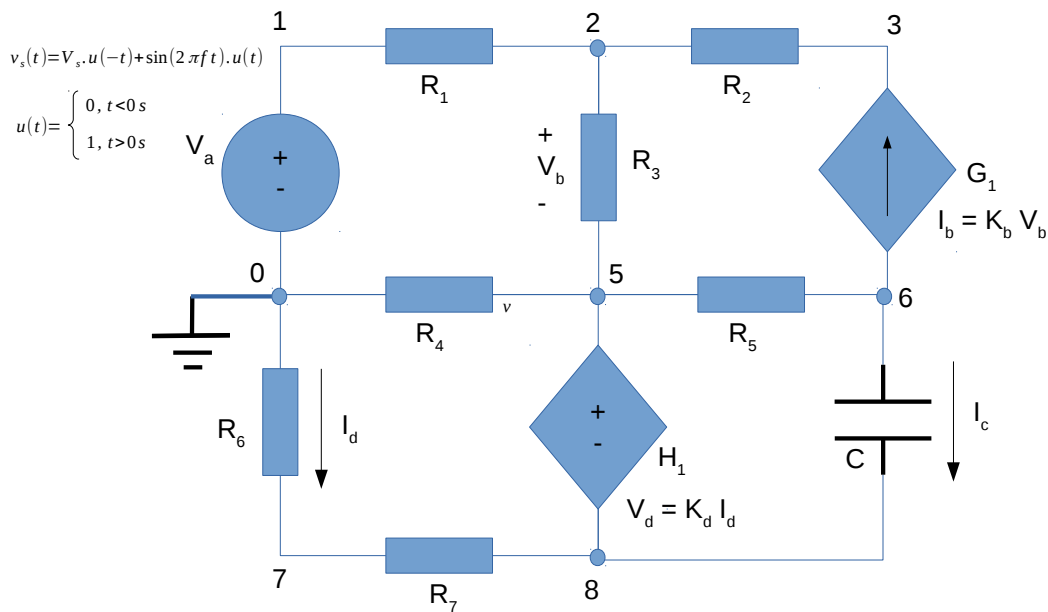
# 1 Introduction

The objective of this laboratory assignment is to study an RC circuit as described in Figure ??.



07/04/2021

TCFE/ DEEC/ Instituto Superior Técnico

1

Figure 1: T2 RC circuit.

The objective of this laboratory assignment is to study the circuit detailed in figure 1, looking at its operation in function of the sinusoidal voltage source  $v_s$ .

In Section 2 we will perform the Theoretical Analysis, analogous to the previous section, we will do the analysis of the circuit making use of theoretical methods, such as the Thevenin and the Phasor Analysis.

In Section 3 we will perform the Simulation Analysis of the circuit, making use of the NGSpice software. We will simulate the circuit to obtain, among other things, the natural and the forced responses of the circuit.

In Section 4 we shall compare the results obtained in Sections 2 and 3, and comment on the differences (should they exist) and draw our conclusions.

## 2 Theoretical Analysis

The values used in both analysis are the following:

Name	Value
$R_1$	1.007812 $k\Omega$
$R_2$	2.003112 $k\Omega$
$R_3$	3.045036 $k\Omega$
$R_4$	4.178966 $k\Omega$
$R_5$	3.106157 $k\Omega$
$R_6$	2.060902 $k\Omega$
$R_7$	1.006346 $k\Omega$
$V_S$	5.048640 V
$C_n$	1.025026 $\mu F$
$K_b$	7.059582 mS
$K_d$	8.039139 mS

Table 1: Circuit data generated by inputing 86639 to the *t2\_datagen.py* file.

### 2.1 Analysis for $t_1=0$

For  $t_1=0$  we can see that we are working in the steady state, given that in that time interval  $v_S = V_S$ . In a DC circuit, the capacitor charges up to it's full capacity, blocking the flow of electricity. Taking this into account we can replace the capacitor with an open circuit. With this information, and knowing that the the tension in  $V_4$ , since it is connected to ground, we can obtain the following equations.

$$\begin{bmatrix} -1 & 0 & 0 & 0 & 0 & 0 & 0 \\ G_1 & -G_1 - G_2 - G_3 & G_2 & G_3 & 0 & 0 & 0 \\ 0 & -K_b - G_2 & G_2 & K_b & 0 & 0 & 0 \\ G_1 & -G_1 & 0 & -G_4 & 0 & -G_6 & 0 \\ 0 & 0 & 0 & 0 & 0 & G_6 + G_7 & -G_7 \\ 0 & 0 & 0 & -1 & 0 & -G_6 * K_d & 1 \\ 0 & G_3 & 0 & -G_3 - G_4 - G_5 & G_5 & -G_6 & 0 \end{bmatrix} \times \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \end{bmatrix} = \begin{bmatrix} -V_s \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad (1)$$

After solving them with the Octave software, we obtained the following results:

Name	Value
V1	5.048640 V
V2	4.860629 V
V3	4.468710 V
V5	4.888344 V
V6	5.496080 V
V7	-2.026270 V
V8	-3.015705 V
$I(R_1)$	0.186554 mA
$I(R_2)$	0.195655 mA
$I(R_3)$	0.009102 mA
$I(R_4)$	1.169750 mA
$I(R_5)$	0.195655 mA
$I(R_6)$	0.983196 mA
$I(R_7)$	0.983196 mA
$I(V_s)$	0.186554 mA
$I_b$	-0.195655 mA
$I_c$	0.000000 mA
$I(K_d)$	0.983196 mA

Table 2: Nodal Analysis for  $t < 0$  s. Currents are expressed in milliAmpere and Voltages are expressed in Volt.

## 2.2 Equivalent Resistance and Initial Conditions

In order to determine the equivalent resistance we need to determine  $V_X$ , this is, the difference between  $V_6 - V_8$ . This is made to ensure that the voltage in the capacitor is continuous.

Making use of the matrix below:

$$\begin{bmatrix}
 -1 & 0 & 0 & 0 & 0 & 0 & 0 \\
 G1 & -G1 - G2 - G3 & G2 & G3 & 0 & 0 & 0 \\
 0 & -Kb - G2 & G2 & Kb & 0 & 0 & 0 \\
 G1 & -G1 & 0 & -G4 & 0 & -G6 & 0 \\
 0 & 0 & 0 & 0 & 0 & G6 + G7 & -G7 \\
 0 & 0 & 0 & -1 & 0 & -G6 * Kd & 1 \\
 0 & 0 & 0 & 0 & -1 & 0 & 1
 \end{bmatrix}
 \begin{bmatrix}
 V1 \\
 V2 \\
 V3 \\
 V5 \\
 V6 \\
 V7 \\
 V8
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 -V_x
 \end{bmatrix} \quad (2)$$

And knowing that:

$$V_x = V_6 - V_8 \quad (3)$$

$$I_x = \frac{V_6 - V_5}{R_5} + \frac{V_3 - V_2}{R_2} \quad (4)$$

$$R_{eq} = \frac{V_x}{I_x} \quad (5)$$

$$\tau = R_{eq} * C \quad (6)$$

We can obtain the following values:

Name	Value
$V_x$	8.511786 V
$I_x$	2.740295 mA
$R_{Eq}$	3.106157 kΩ
$\tau$	0.003184 s

Table 3: Second nodal analysis and calculations for  $R_{Eq}$  and  $\tau$ . Currents are expressed in *milliAmpere*, Voltages are expressed in *Volt*, Resistances are expressed in *kiloOhm* and Time Constant is expressed in *second*.

## 2.3 Natural Solution

The natural solution doesn't take into account independent power sources. Using  $V_x$  as the initial condition the natural solution can be obtained with the following equation

$$V_{6n}(t) = V_x e^{(-\frac{t}{\tau})} \quad (7)$$

After computing this data on Octave, we can plot the results of the interval  $[0, 20]$ ms.

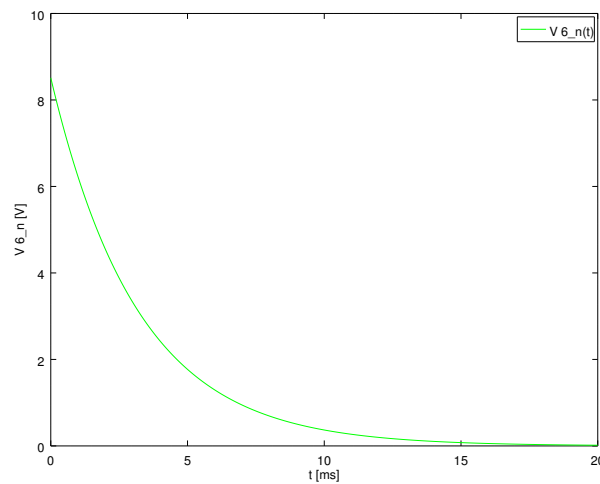


Figure 2: Natural solution  $V_{6n}$  in the interval  $[0, 20]$  ms plot.

## 2.4 Forced Solution

In order to obtain the forced solution we must be able to solve the following equation.

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ -G1 & G1 + G2 + G3 & -G2 & -G3 & 0 & 0 & 0 \\ 0 & Kb + G2 & -G2 & -Kb & 0 & 0 & 0 \\ -G1 & G1 & 0 & G4 & 0 & G6 & 0 \\ 0 & 0 & 0 & 0 & 0 & -G6 - G7 & G7 \\ 0 & 0 & 0 & 1 & 0 & G6 * Kd & -1 \\ 0 & -G3 & 0 & G3 + G4 + G5 & -G5 - jwC & G6 & jwC \end{bmatrix} \begin{bmatrix} V1 \\ V2 \\ V3 \\ V5 \\ V6 \\ V7 \\ V8 \end{bmatrix} = \begin{bmatrix} -j \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad (8)$$

The solution to this system is presented in the table below:

Name	Complex Amplitude [V]	Phase [Degrees]
$V_1$	1.000000	-90.000000
$V_2$	0.962760	-90.000000
$V_3$	0.885131	-90.000000
$V_5$	0.968250	-90.000000
$V_6$	0.599056	98.067060
$V_7$	0.401350	90.000000
$V_8$	0.597330	90.000000

Table 4: Nodal analysis for phasor voltage in forced state.

These values are needed to determine the forced solution  $V_{6f}$ , which is given by the following formula:

$$V_{6f}(t) = V_{6r} \cos(\omega t + V_{6\phi}); \quad (9)$$

Where

$$\omega = 2\pi f; \quad (10)$$

## 2.5 Final Total Solution

The final total solution  $V_6(t)$  is achieved by superimposing the natural and forced solutions.

$$V_6(t) = V_{6n}(t) + V_{6f}(t); \quad (11)$$

By converting the phasors to real time functions for  $f = 1kHz$  and superimposing the natural and forced solutions, we can plot both  $V_S(t)$  and  $V_6(t)$  in the interval  $[-5, 20] ms$ , as shown in the figure below:

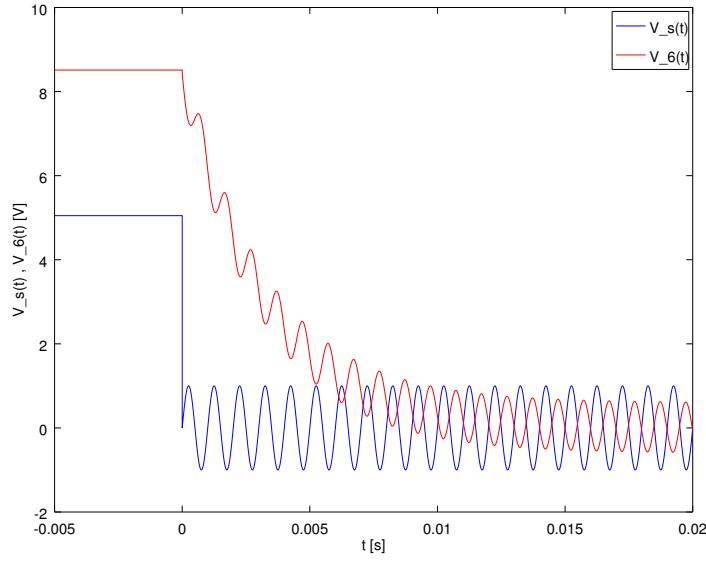


Figure 3: Total solution of  $V_6$  and  $V_s$  plot.

As expected, both curves shown in Figure ?? are constant for  $t < 0$  s. For  $t > 0$  s, we can see an evident negative exponential behavior and an induced frequency in  $V_6$ .

## 2.6 Frequency Responses

As we can see in the figure below, for low frequencies every voltage is in phase. The capacitor is given enough time to charge up.

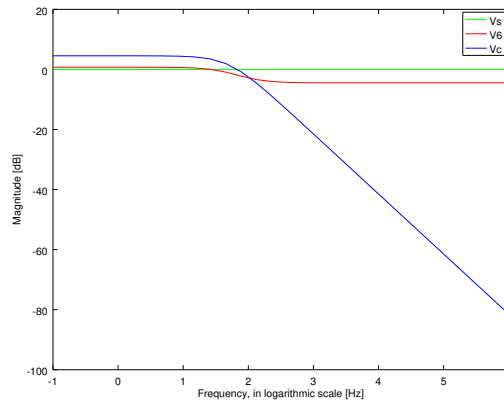


Figure 4: Total solution of  $V_6$  compared to  $V_s$

The circuit being analysed can be used as a low-pass filter. This means that, for low frequencies, the capacitor has time to charge up to almost the same voltage provided as input (it approximates to an open-circuit behavior), which translates to a proximity in phase between the voltage in the capacitor and the voltage source. Having said that, high frequencies, on the other hand, will give the capacitor a small time to charge up before a change in the input direction occurs (it approximates to a short-circuit behavior), which translates to a growing difference in phase between the voltage in the capacitor and the voltage source. This difference of phase is noticeable for frequencies greater than the cut-off frequency,  $f_c$ , which is given by  $f_c = \frac{1}{2\pi\tau}$ . In this particular case, the cut-off frequency value is approximately 50 Hz. This is why we see



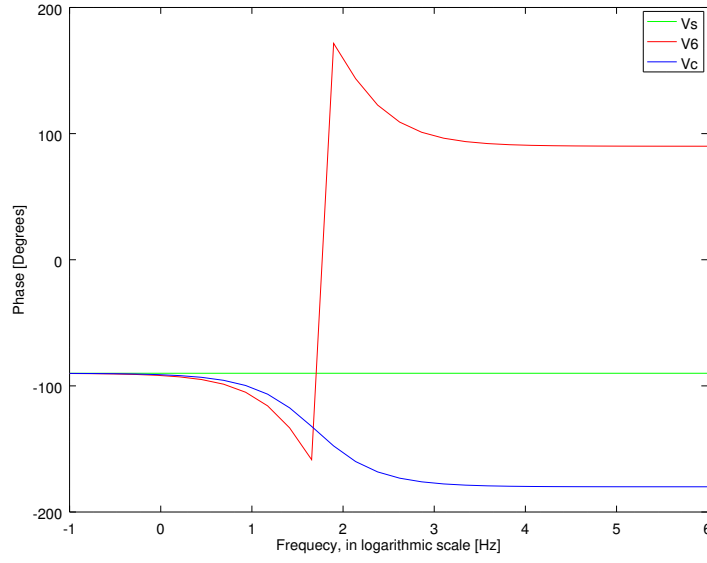


Figure 5: Variation of the voltage magnitudes of  $V_s$ ,  $V_6$  and  $V_c$  in function of frequency

a significant voltage drop in Fig ?? at around  $10\text{ Hz}$  and  $10^2\text{ Hz}$ . The phase difference also starts to increase in that same range, as seen in Fig ??.

By simplifying this circuit to an equivalent one composed by a voltage source, capacitor and equivalent resistor, we reach the following equations that help us to better comprehend the magnitude drop and the phase difference rise with the increase of frequency:

$$V_c = \frac{V_s}{\sqrt{1 + (R_{Eq} \times C \times 2\pi \times f)^2}} \quad (12)$$

$$\phi_{V_c} = -\frac{\pi}{2} + \arctan(R_{Eq} \times C \times 2\pi \times f) \quad (13)$$

### 3 Simulation Analysis

In this section we analysed the circuit making use of the NGSpice software. Given that this circuit has a sinusoidal voltage source, the current that flows through the circuit components varies with time. As such, in order to simulate the circuit's total response we must run a transient analysis. We also ran an operating point analysis for  $t < 0$  and  $t = 0$ .

#### 3.1 Operating Point Analysis

Table ?? shows the simulated operating point results for  $t < 0$  s, where it's assumed that no current flows through the capacitor (open circuit). Table ?? shows the simulated operating point results for  $t = 0$  s, where  $V_S$  is short-circuited and the capacitor is replaced with a voltage source  $V_x = V(6) - V(8)$  (with  $V(6)$  and  $V(8)$  as obtained in Table ??).

Name	Value [A or V]
v(1)	0.000000e+00
v(2)	1.662312e-15
v(3)	5.127494e-15
v(5)	1.417269e-15
v(6)	8.511786e+00
v(7)	-8.18711e-16
v(8)	-1.77636e-15
v(9)	-8.18711e-16

Table 5: Operating point data for  $t < 0$  s. A variable preceded by @ is of type Current and is expressed in Ampere; other variables are of type Voltage and are expressed in Volt.

Name	Value [A or V]
v(1)	0.000000e+00
v(2)	1.662312e-15
v(3)	5.127494e-15
v(5)	1.417269e-15
v(6)	8.511786e+00
v(7)	-8.18711e-16
v(8)	-1.77636e-15
v(9)	-8.18711e-16

Table 6: Operating point data for  $t = 0$  s. A variable preceded by @ is of type Current and is expressed in Ampere; other variables are of type Voltage and are expressed in Volt.

Compared to the theoretical analysis results, one notices that the simulated data matches almost perfectly the theoretical values. This is expected, as the circuits being simulated in both scenarios are exclusively composed by linear components.

## 3.2 Transient Analysis

### 3.2.1 Natural Response

Figure ?? shows the plot of the simulated transient analysis results in the interval  $[0, 20] \text{ ms}$ , using the boundary conditions of  $V(6)$  and  $V(8)$  as determined before. Once again, the simulation data matches with the theoretical natural response prediction, and one can clearly see the negative exponential behavior of  $V(6)$ , as was expected.

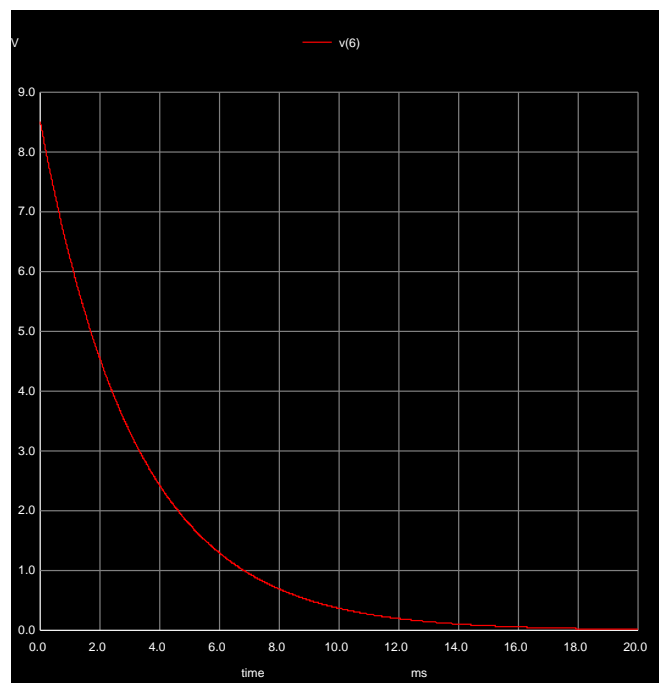


Figure 6: Natural response of  $V_6$  in the interval  $[0, 20] \text{ ms}$ .

### 3.2.2 Total Response

Figure ?? shows the plot of the simulated transient analysis results in the interval  $[0, 20] \text{ ms}$ , by using  $V_S(t)$  as given in Figure ?? and  $f = 1 \text{ kHz}$ . Once again, the simulation data matches with the theoretical total response prediction, as was expected.

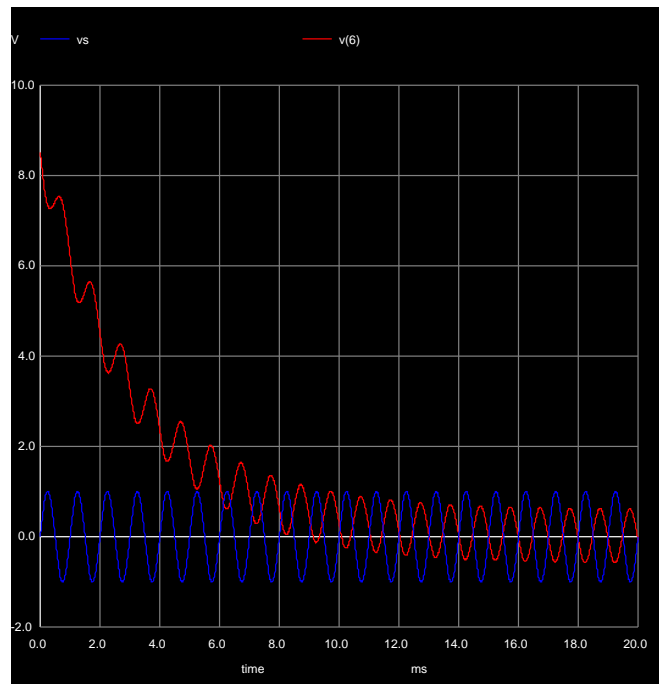


Figure 7: Total response of  $V_6$  and  $V_S$  in the interval  $[0, 20] \text{ ms}$ .

### 3.3 Frequency Analysis

In this section, the frequency response in node 6 is simulated, with the frequency in logscale, magnitude in  $dB$  and phase in  $degrees$ , for the frequency range of  $0.1\text{ Hz}$  to  $1\text{ MHz}$ .

#### 3.3.1 Magnitude Response

Figure ?? shows the magnitude of the frequency response for the circuit under analysis. Compared to the theoretical analysis results, one notices a clear match between plots. Thus, the reasons for how  $V(6)$  and  $V_S$  differ from each other are the same as explained in the theoretical analysis above.

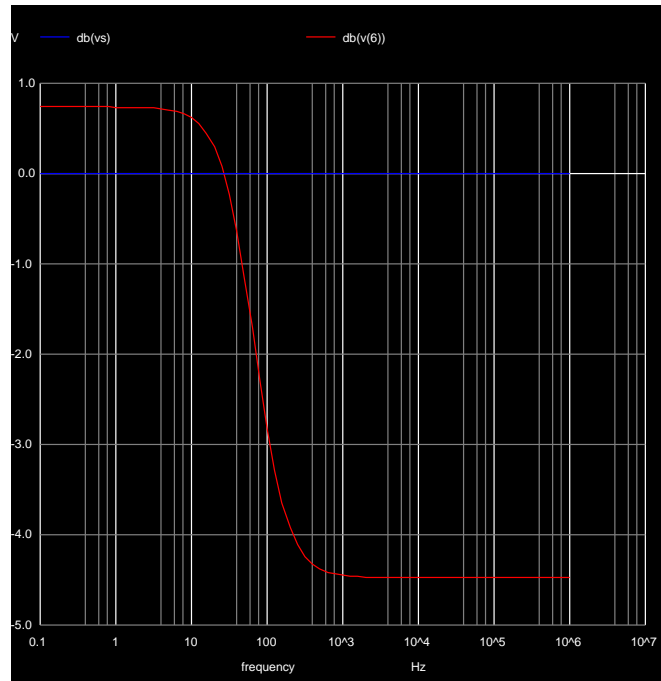


Figure 8: Magnitude of frequency response of  $V(6)$  and  $V_S$  plot.

### 3.3.2 Phase Response

Figure ?? shows the magnitude of the frequency response for the circuit under analysis. Compared to the theoretical analysis results, one notices a clear match between plots. Thus, the reasons for how  $V(6)$  and  $V_S$  differ from each other are the same as explained in the theoretical analysis above.

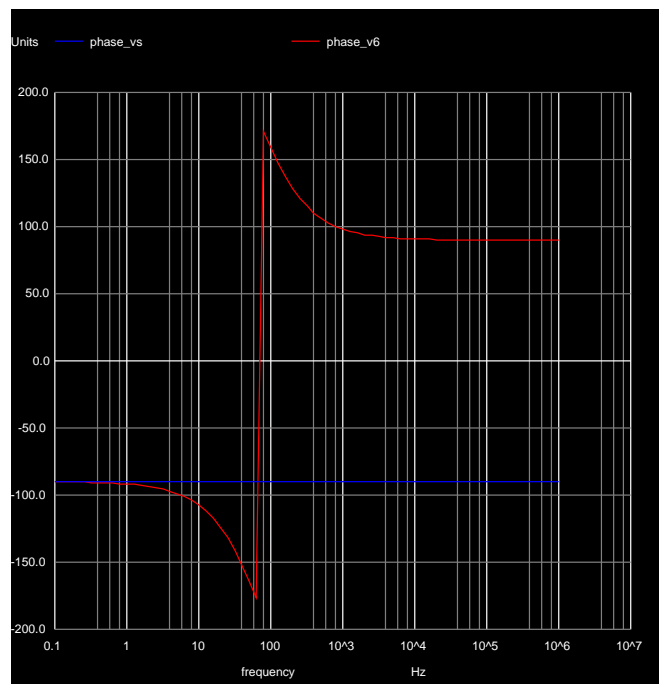


Figure 9: Phase response of  $V(6)$  and  $V_S$  plot.

## 4 Conclusion

In this laboratory assignment the objective of analysing an RC circuit has been achieved with success.

The theoretical estimates were compared with the simulation results, yielding very similar results. The plots obtained from performing the nodal method in GNU Octave and the simulation in NGSpice are mostly identical, with errors being of such low order of magnitude that they become negligible, and are most likely attributable to rounding errors. This outcome was expected, since the circuit is composed of linear components, and hence NGSpice likely used the same methods as Octave did in the theoretical part. Because the results are coherent and within expectation, we consider this task to be successful.